



EECS 151/251A

Spring 2019

Digital Design and Integrated Circuits

Instructor:

John Wawrzynek

Lecture 16



Memory Circuits




General Latch Design

Storage principles


- Hardwired (Read-only-memory- ROM)
- Programmable
 - *Volatile*
 - Feedback to hold state while power is on
 - *Non-volatile*
 - Persistent state without power supplied

Volatile Storage Mechanisms


Static - feedback

 

Dynamic - charge

 


Basic Static Storage Element

 

- If D is high, D_b will be driven low
 - Which makes D stay high
- Positive feedback
- Tolerant to noise and other small disturbances



A Static Latch

 

Access transistor must be able to overpower the feedback.

Addressing the write problem

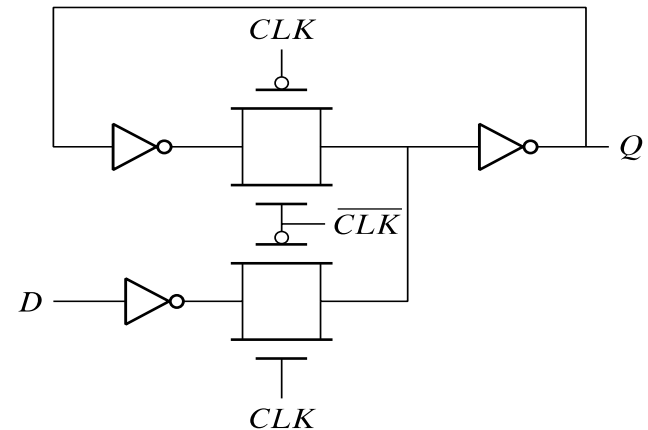 Use the clock as a decoupling signal,
that distinguishes between the transparent and opaque states



Implemented with a MUX.




Memories

Semiconductor Memory Classification


Read-Write Memory		Non-Volatile Read-Write Memory	Read-Only Memory
Random Access	Non-Random Access	EPROM E ² PROM FLASH	Mask-Programmed Programmable (PROM)
SRAM DRAM	FIFO LIFO Shift Register CAM		

Storage Mechanisms

Static (SRAM)

 


Dynamic (DRAM)

 

Memory Architecture Overview

 - ❑ **Word lines** used to select a row for reading or writing
- ❑ **Bit lines** carry data to/from periphery
- ❑ **Core aspect ratio** keep close to 1 to help balance delay on word line versus bit line
- ❑ **Address bits** are divided between the two decoders
- ❑ **Row decoder** used to select word line
- ❑ **Column decoder** used to select one or more columns for input/output of data







Memory - SRAM

Memory Cells

 
Complementary data values are written (read) from two sides




Cells stacked in 2D to form memory core.

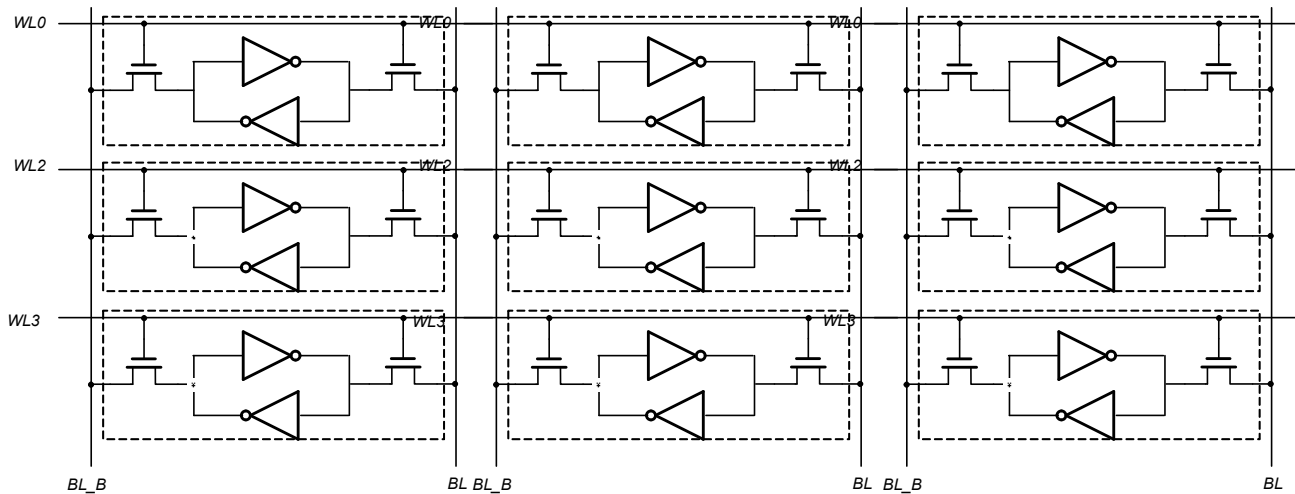

SRAM read/write operations

 


6-Transistor CMOS SRAM Cell

 

SRAM Operation - Read


 
1. Bit lines are “pre-charged” to VDD
2. Word line is driven high (pre-charger is turned off)
3. Cell pulls-down one bit line
4. Differential sensing circuit on periphery is activated to capture value on bit lines.



During read \overline{Q} will get pulled up when WL first goes high, but ...

- Reading the cell should not destroy the stored value


CMOS SRAM Analysis (Read)

 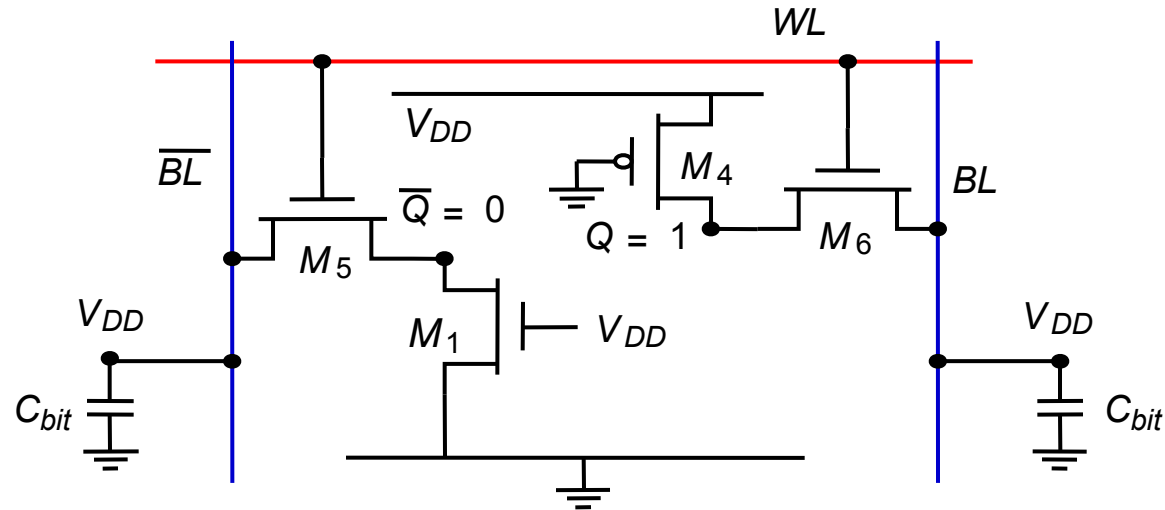

$$CR = \frac{W_1/L_1}{W_5/L_5}$$



SRAM Operation - Write

 1. Column driver circuit on periphery differentially drives the bit lines
2. Word line is driven high (column driver stays on)
3. One side of cell is driven low, flips the other side



For successful write the access transistor needs to overpower the cell pullup

CMOS SRAM Analysis (Write)

 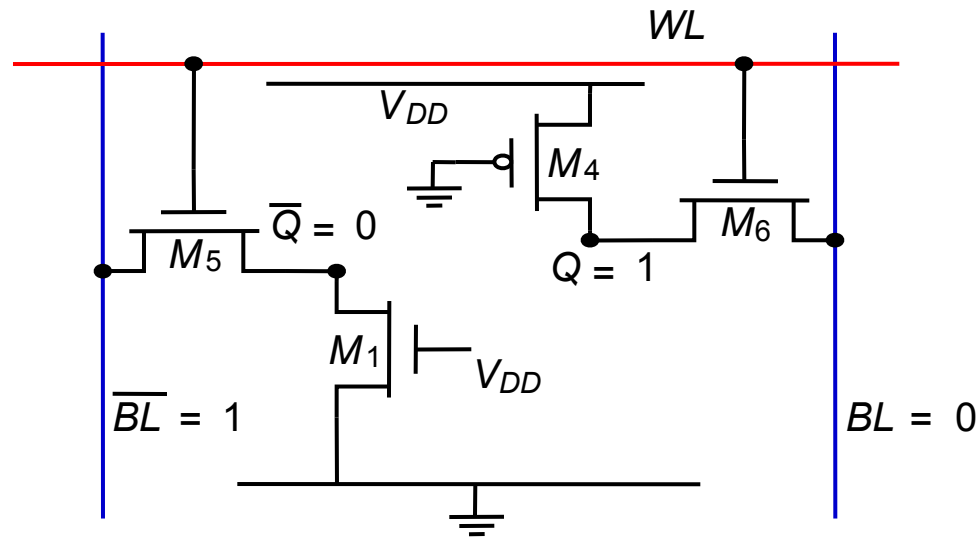


*Size width ratio
between PMOS
pull-up and NMOS
access*

$$\frac{W_4/L_4}{W_6/L_6}$$

6T-SRAM — Layout


 
V_{DD} and GND: in M1
Bitlines: M2
Wordline: poly-silicon



65nm SRAM

□ ST/Philips/Motorola

Access Transistor

  




Memory Periphery

Periphery

- ❑ Decoders
- ❑ Sense Amplifiers
- ❑ Input/Output Buffers
- ❑ Control / Timing Circuitry

Row Decoder

 - Expands L-K address lines into 2^{L-K} word lines



- Example: decoder for 8Kx8 memory block
 - core arranged as 256x256 cells
 - Need 256 AND gates, each driving one word line

Row Decoders

(N)AND Decoder


$$WL_0 = A_0 A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 A_9$$

$$WL_{511} = \bar{A}_0 A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 A_9$$

NOR Decoder

$$WL_0 = \overline{A_0 + A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8 + A_9}$$
 
$$WL_{511} = \overline{A_0 + \bar{A}_1 + \bar{A}_2 + \bar{A}_3 + \bar{A}_4 + \bar{A}_5 + \bar{A}_6 + \bar{A}_7 + \bar{A}_8 + \bar{A}_9}$$



Collection of 2^K logic gates, but need to be dense and fast.

Predecoders


$\overline{a_5}$	$\overline{a_4}$	$\overline{a_3}$	$\overline{a_2}$	$\overline{a_1}$	$\overline{a_0}$
$\overline{a_5}$	$\overline{a_4}$	$\overline{a_3}$	$\overline{a_2}$	$\overline{a_1}$	a_0
$\overline{a_5}$	$\overline{a_4}$	$\overline{a_3}$	$\overline{a_2}$	a_1	$\overline{a_0}$
$\overline{a_5}$	$\overline{a_4}$	$\overline{a_3}$	$\overline{a_2}$	a_1	a_0
$\overline{a_5}$	$\overline{a_4}$	$\overline{a_3}$	a_2	$\overline{a_1}$	$\overline{a_0}$
$\overline{a_5}$	$\overline{a_4}$	$\overline{a_3}$	a_2	$\overline{a_1}$	a_0
$\overline{a_5}$	$\overline{a_4}$	$\overline{a_3}$	a_2	a_1	$\overline{a_0}$
$\overline{a_5}$	$\overline{a_4}$	$\overline{a_3}$	a_2	a_1	a_0

•
•
•


a_5	a_4	a_3	a_2	$\overline{a_1}$	$\overline{a_0}$
a_5	a_4	a_3	a_2	$\overline{a_1}$	a_0
a_5	a_4	a_3	a_2	a_1	$\overline{a_0}$
a_5	a_4	a_3	a_2	a_1	a_0

- ❑ Use a single gate for each of the shared terms
 - E.g., from $a_1, \overline{a_1}, a_0, \overline{a_0}$ generate four signals:
 - $\overline{a_1} \overline{a_0}, \overline{a_1} a_0, a_1 \overline{a_0}, a_1 a_0$
- ❑ In other words, we are decoding smaller groups of address bits first
 - And using the “predecoded” outputs to do the rest of the decoding

Predecoder and Decoder

 


Column “Decoder”

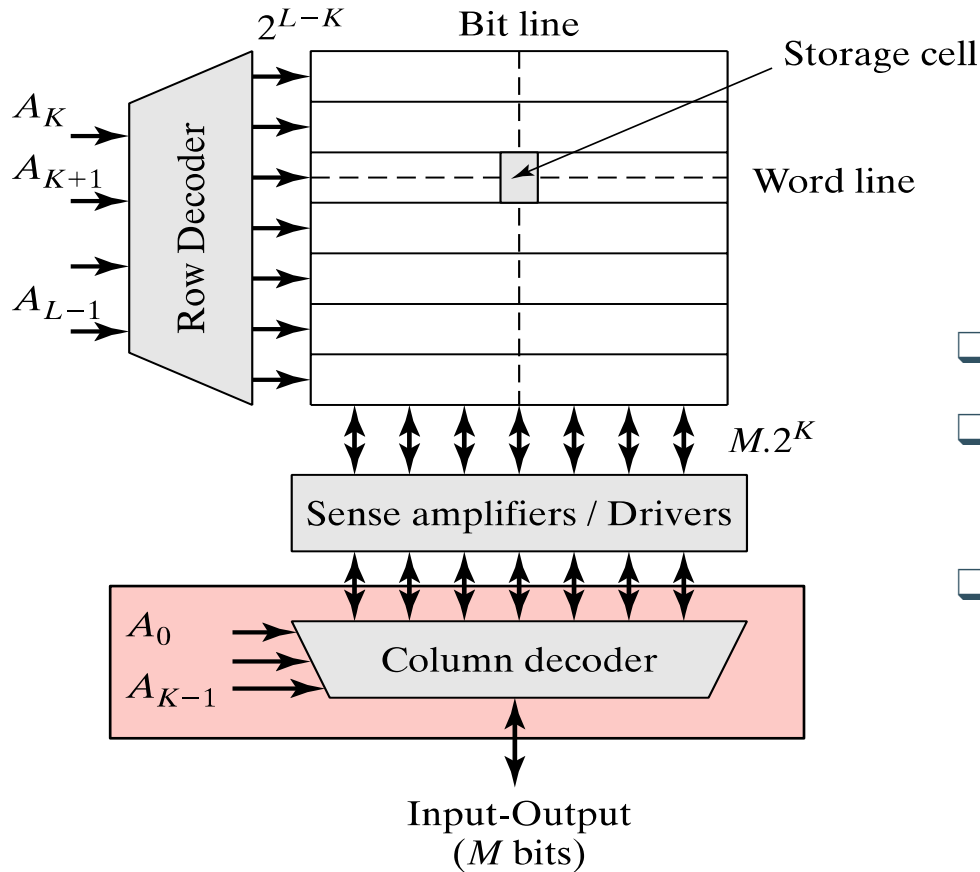

- ❑ Is basically a multiplexer
- ❑ Each row contains 2^K words each M bit wide.
- ❑ Bit of each of the 2^K are interleaved
 - ❑ ex: $K=2$, $M=8$

$d_7 c_7 b_7 a_7 d_6 c_6 b_6 a_6 d_5 c_5 b_5 a_5 d_4 c_4 b_4 a_4 d_3 c_3 b_3 a_3 d_2 c_2 b_2 a_2 d_1 c_1 b_1 a_1 d_0 c_0 b_0 a_0$

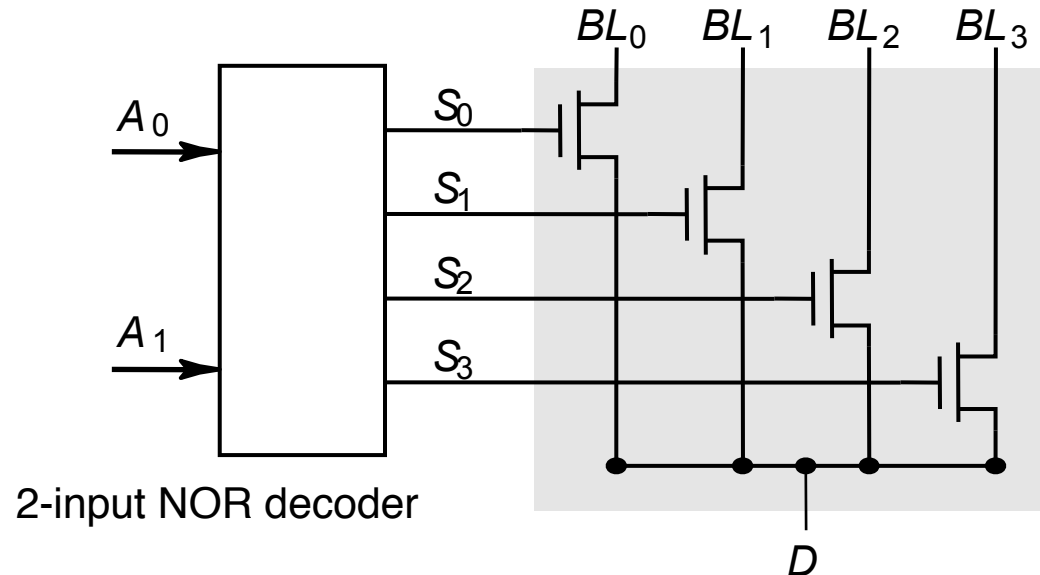4-input pass-transistor based Column Decoder



decoder shared across all $2^K \times M$ row bits

Advantages: speed (t_{pd} does not add to overall memory access time)

Only one extra transistor in signal path


Sense Amplifiers

Sense Amplifiers


$$\tau_p = \frac{C \cdot \Delta V}{I_{av}}$$

large \rightarrow $C \cdot \Delta V$ \leftarrow make as small as possible
 I_{av} \leftarrow small

Idea: Use Sense Amplifier

 


Differential Sense Amplifier

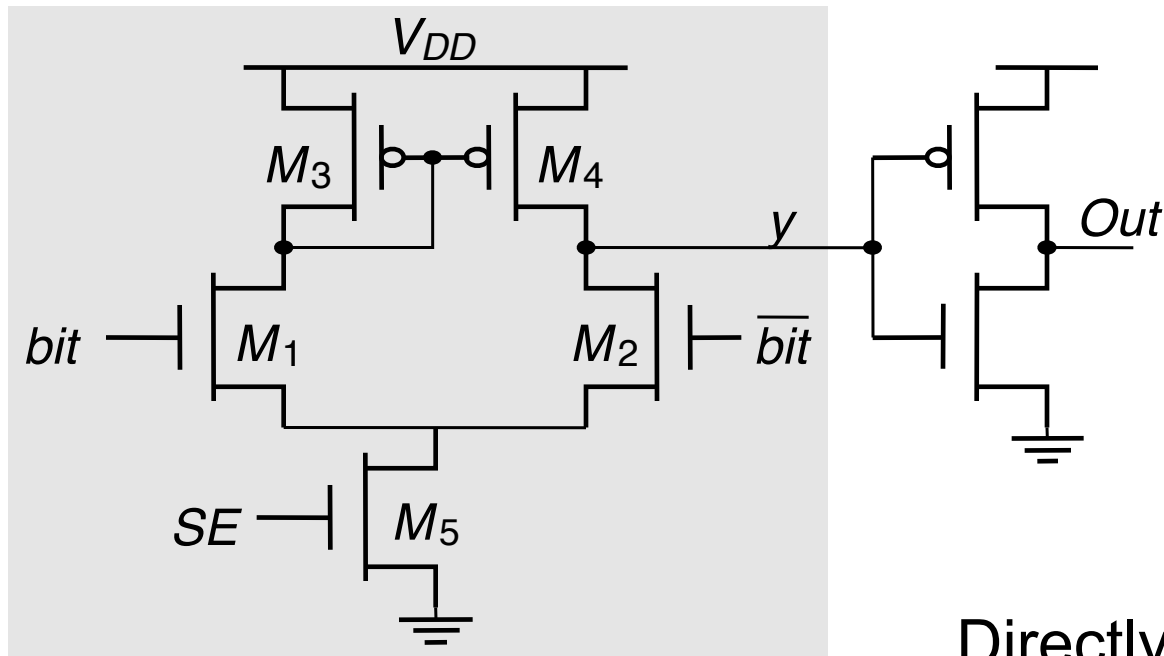


Directly applicable to
SRAMs

Differential Sensing — SRAM

 

(a) SRAM sensing scheme


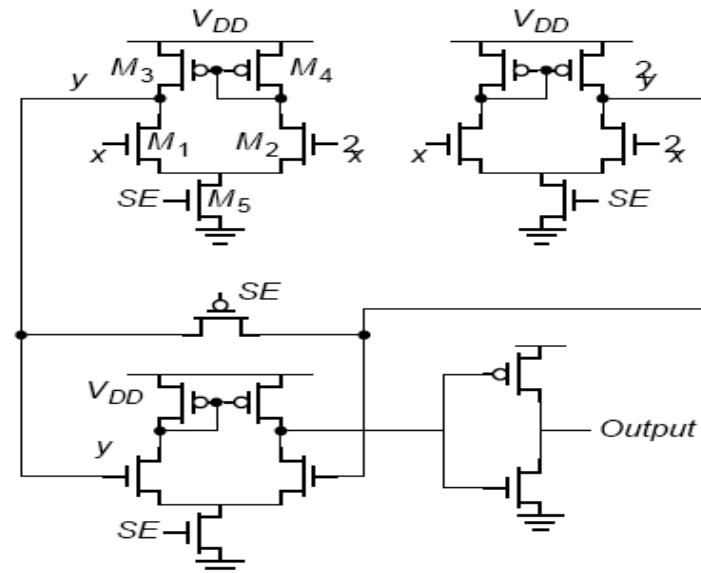


(b) two stage differential amplifier



Memory - DRAM

3-Transistor DRAM Cell

  


No constraints on device ratios

Reads are non-destructive

Value stored at node X when writing a “1” = $V_{WWL} - V_{Tn}$

Can work with a normal logic IC process

1-Transistor DRAM Cell

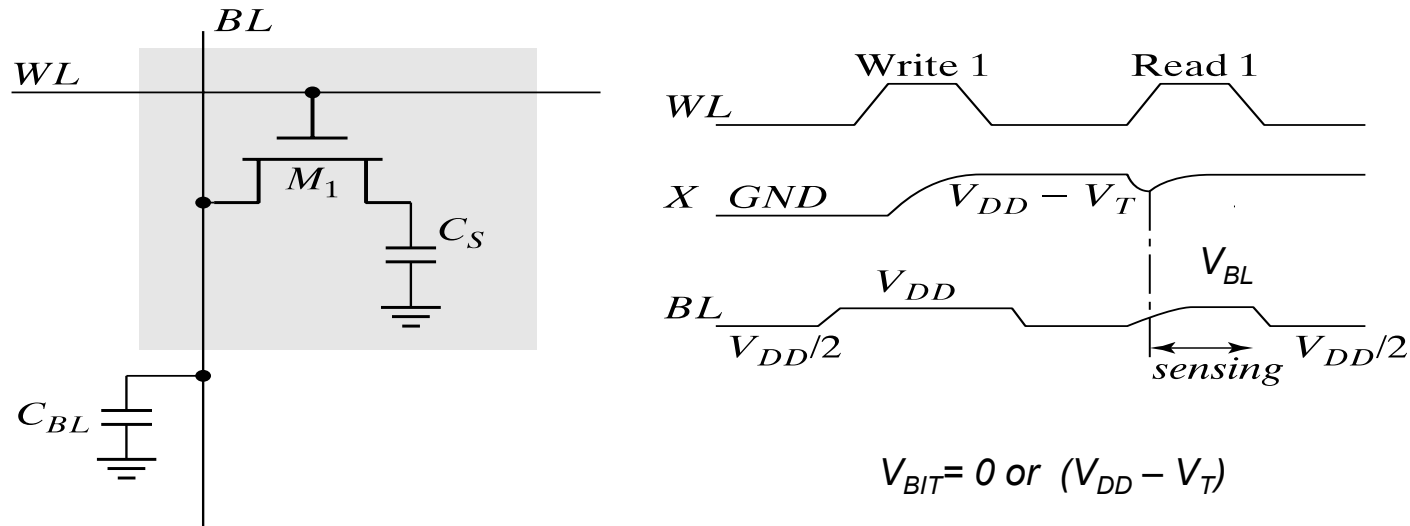


Write: C_S is charged or discharged by asserting WL and BL.

Read: Charge redistribution takes place between bit line and storage capacitance

$C_S \ll C_{BL}$ Voltage swing is small; typically around 250 mV.


- ❑ To get sufficient C_S , special IC process is used
- ❑ Cell reading is destructive, therefore read operation always is followed by a write-back
- ❑ Cell loses charge (leaks away in ms - highly temperature dependent), therefore cells occasionally need to be “refreshed” - read/write cycle

Latch-Based Sense Amplifier (DRAM)

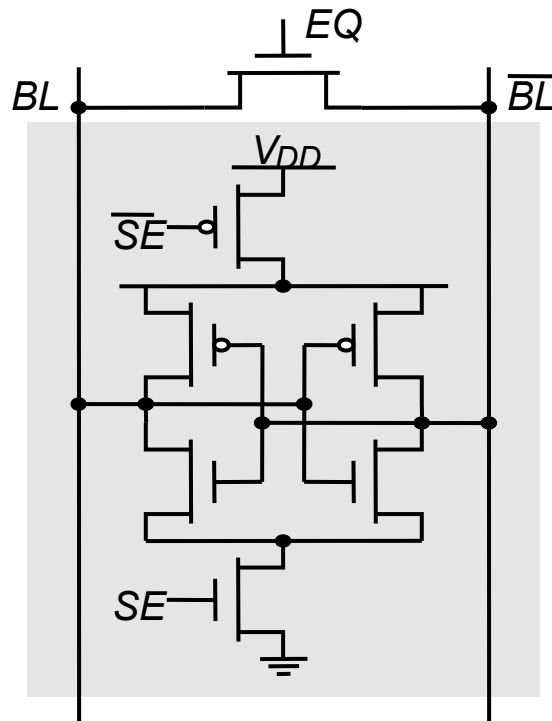

- Initialized in its meta-stable point with EQ
- Once adequate voltage gap created, sense amp enabled with SE
- Positive feedback quickly forces output to a stable operating point.

Advanced 1T DRAM Cells

 

Cell Plate Si

Capacitor Insulator


Storage Node Poly

2nd Field Oxide

Refilling Poly

Si Substrate

Trench Cell

 

Stacked-capacitor Cell




Multi-ported memory


Multi-ported Memory

□ Motivation:

 - Consider CPU core register file:
 - 1 read or write per cycle limits processor performance.
 - Complicates pipelining. Difficult for different instructions to simultaneously read or write regfile.
 - Common arrangement in pipelined CPUs is 2 read ports and 1 write port.




- I/O data buffering:

 


- dual-porting allows both sides to simultaneously access memory at full bandwidth.

Dual-ported Memory Internals

 - Add decoder, another set of read/write logic, bits lines, word lines:



- Example cell: SRAM

 

- Repeat everything but cross-coupled inverters.
- This scheme extends up to a couple more ports, then need to add additional transistors.